

LED Short Leg (-) to Breadboard (-)
LED Long Leg (+) to 1K Resistor to (Digital) Pin 13

VCC (+) to Breadboard (+)
Trig to (Digital) Pin 8
Echo to (Digital) Pin 7
GND (-) to Breadboard (-)

5V to Breadboard (+)
GND to Breadboard (-)

